


Assignment-VIII

Experiment Title:- Design of n-bit simple ALU design using MUX


Apparatus Required:- IC trainer Kit, Connecting wires, IC-4539 AND gates, (IC-4081), NOT Gate (IC-4069), OR gate (IC-4071) and XOR Gate (IC-4070).

Theory:- Logical microoperations are very useful for manipulating individual bits or a portion of a word stored in a registers. They can be used to change the bit values, delete group of bits or insert new bit values into a register. These microoperation require different logic gates to be inserted for each bit or pair of bits in the registers to perform the required operation.

Pin Diagram:-

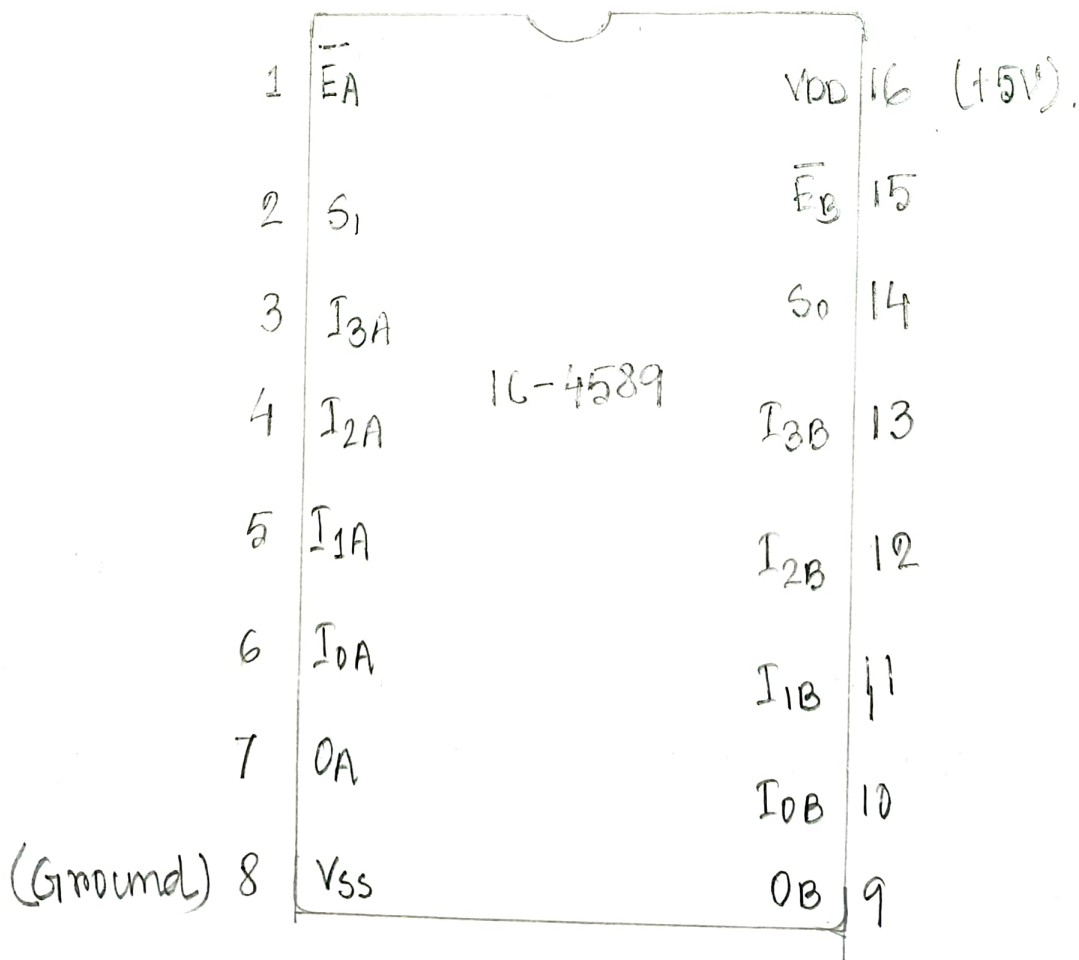

Circuit Diagram:-

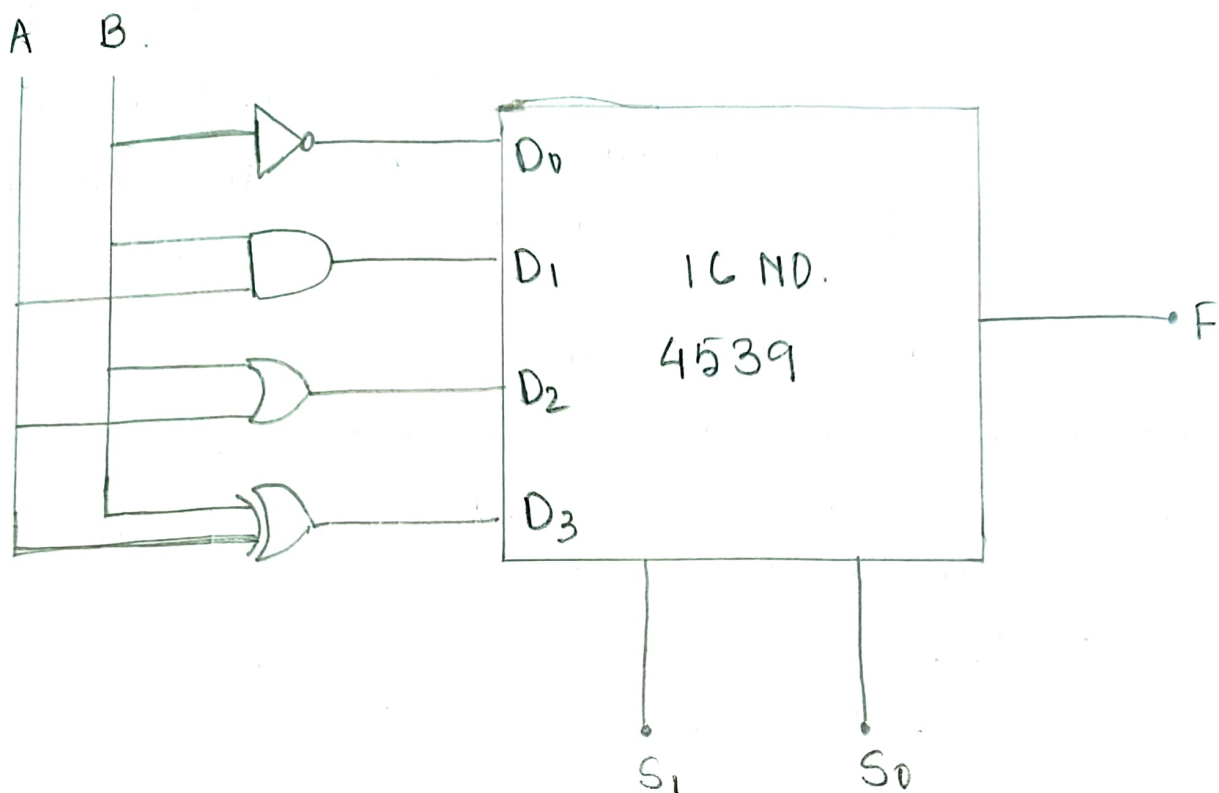

Truth Table:-

Select lines		Input		Output	Operational
S_1	S_0	A_i	B_i	F_i	
0	0	0	0	1	NOT
0	1	0	1	0	AND
1	0	1	0	1	OR
1	1	1	1	0	XOR

Conclusion:- Implementation of n-bit simple ALU is designed and its truth table is verified..